

Logic Synthesis and CMOS Technology

Reminders:

- Quiz 1 on Thu March 5th 7:30-9:30pm, covers lectures L1-L7 and labs 1-2.
- See piazza / course website for exam rooms
- Quiz review: Tue March 3rd 7:30-9:30pm in 6-120.

Recap: Logic Optimization

- In practice, **tools** use Boolean simplification and other techniques to synthesize a circuit that meets certain area, delay, and power goals:


High-level circuit specification
(e.g., Boolean algebra, Minispec)

Standard cell library
(set of gates and their
physical characteristics)

Synthesis
tool


Optimized circuit
implementation
(using standard
cell library gates)

Optimization goals
(area/delay/power)

 

Logic Synthesis (Continued): Other Common Gates


- XOR (Exclusive-OR)

 


A	B	Z
0	0	0
0	1	1
1	0	1
1	1	0

- Inverting logic

NAND

 


NOR

 

Universal Building Blocks

- NANDs and NORs are universal:

 

- Any logic function can be implemented using only NANDs (or, equivalently, NORs)

Standard Cell Library


- Library of gates and their physical characteristics
- Example:

Gate	Delay (ps)	Area (μ^2)
Buffer	40	20
Inverter	20	10
AND2	50	25
NAND2	30	15
OR2	55	26
NOR2	35	16
AND4	90	40
NAND4	70	30
OR4	100	42
NOR4	80	32

Observations:

- In current technology (CMOS), inverting gates are faster and smaller
- Delay and area grow with number of inputs


Design Tradeoffs: Delay vs Size

 

AND4:


$$t_{PD} = 90 \text{ ps, size} = 40\mu^2$$
 
$$A \wedge B \wedge C \wedge D = (\neg(A \wedge B) \vee \neg(C \wedge D))$$



NAND4 + INV:
 
$$t_{PD} = 90 \text{ ps, size} = 40\mu^2$$




Demorgan's Laws: $\overline{A \cdot B} = \overline{A} + \overline{B}$
 $\overline{A} + \overline{B} = \overline{A \cdot B}$

2*NAND2 + NOR2:


$$t_{PD} = 1 \text{ NAND2} + \text{NOR2} = 65 \text{ ps,}$$
$$\text{size} = 2 \text{ NAND2} + \text{NOR2} = 46\mu^2$$

 Example: Mapping a Circuit to a Standard Cell Library

Find an implementation of a circuit, e.g.,



 
Using gates from a standard cell library, e.g.,



That optimizes for some goal, e.g., minimum area

Example: Mapping a Circuit to a Standard Cell Library


Possible implementations:

 

$$7 \text{ NAND2 (3)} = 21$$

$$5 \text{ INV (2)} = 10$$

Total area cost: 31

 

$$2 \text{ INV} = 4$$

$$2 \text{ NAND2} = 6$$

$$1 \text{ NAND3} = 4$$

$$1 \text{ NAND4} = 5$$


Total area cost: 19

Logic Optimization Takeaways

- Synthesizing an optimized circuit is a very complex problem
 - Boolean simplification
 - Mapping to cell libraries with many gates
 - Multidimensional tradeoffs (e.g., minimize area-delay-power product)
- Infeasible to do by hand for all but the smallest circuits!
- Instead, hardware designers write circuits in a **hardware description language**, and use a **synthesis tool** to derive optimized implementations

CMOS Technology

A Deep Dive Into a Chip


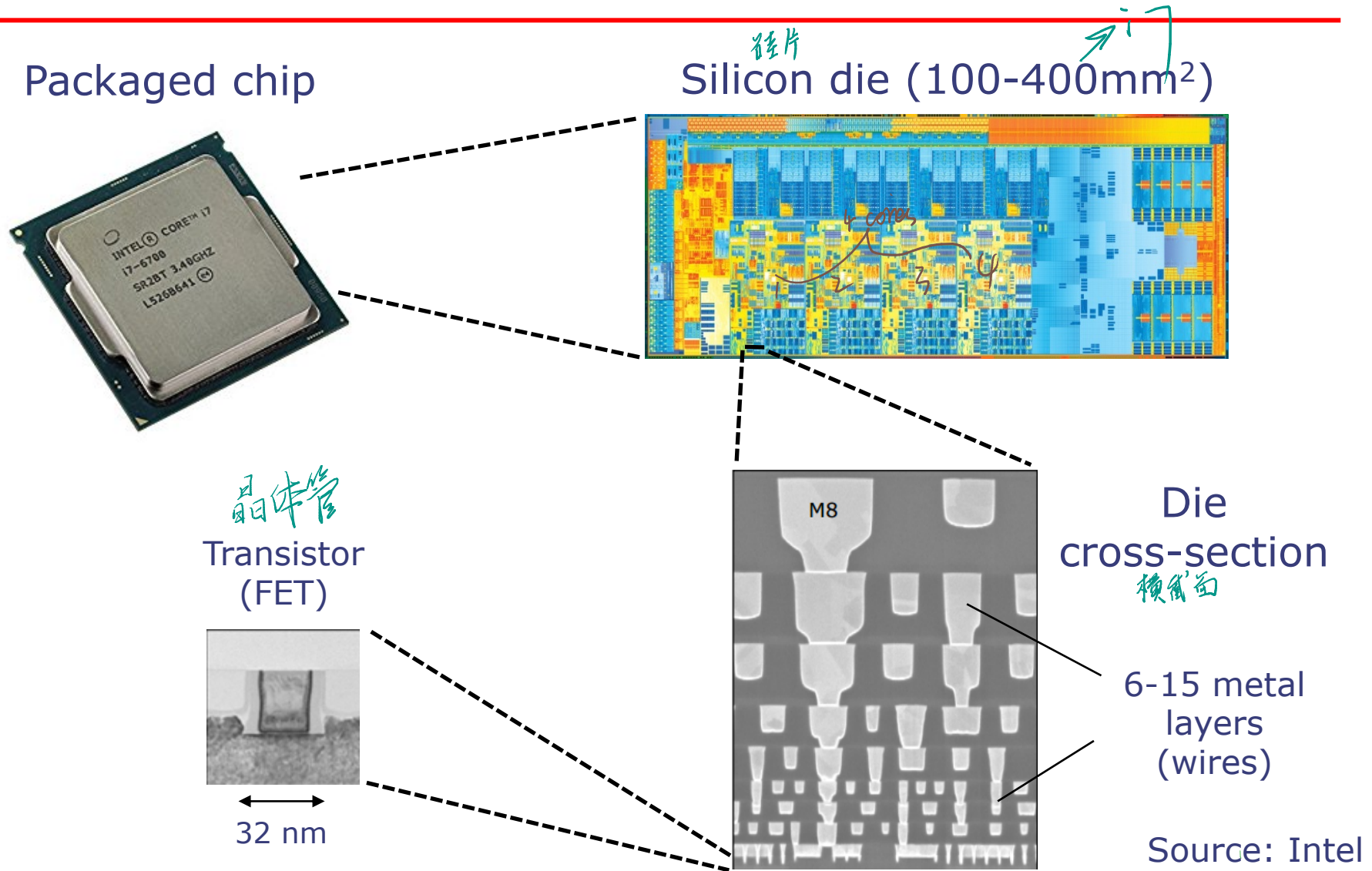


Field-Effect Transistors (FETs)

场效应晶体管

- Nearly all digital systems are built using field-effect transistors, which are **voltage-controlled switches**

  - FETs come in two varieties: nFET and pFET





A high voltage at gate ($G=1$)
creates conducting path
between source and drain

A low voltage at gate ($G=0$)
creates conducting path
between source and drain

Labeling Source and Drain

  
- There is no physical difference between source and drain, called the **diffusion terminals** 扩散端
- By convention, we label diffusion terminals as source or drain depending on their voltages:
 - On nFETs, source = diffusion terminal at lower voltage
 - On pFETs, source = diffusion terminal at higher voltage



- This convention lets us define the behavior of FETs using the voltage between gate and source


FET Switching Model

 - FETs have a **threshold voltage** V_{TH}
- nFET is ON if the voltage between **gate** and **source** V_{GS} exceeds V_{TH} , OFF otherwise
- pFET is ON if the voltage between **source** and **gate** V_{SG} exceeds V_{TH} , OFF otherwise





- This is a very simplified model, but it is sufficient to build logic gates

What Does This Circuit Compute?

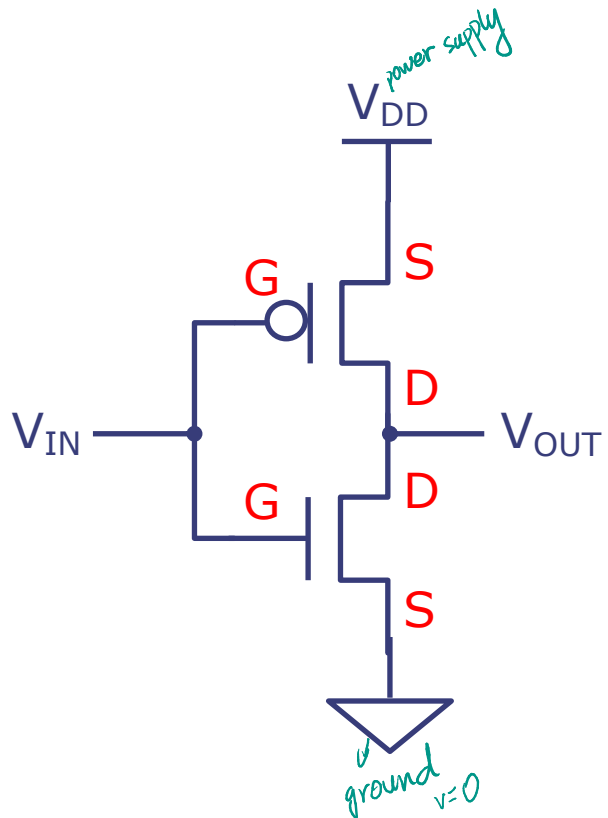

CMOS inverter

  


IN	OUT
0	1
1	0

Note on Terminology


- MOSFETs (metal-oxide-semiconductor field-effect transistors) are the most common type of FET
- nFET and pFET are sometimes abbreviated as nMOS and pMOS 縮写的
- CMOS stands for complementary MOS

What Does This Circuit Compute?

 

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0


CMOS NAND gate

 

CMOS Logic

- CMOS gates have **complementary** pullup and pulldown networks, i.e., the pullup is on when the pulldown is off and vice versa


pullup	pulldown	F(inputs)
on	off	driven "1"
off	on	driven "0"
on	on	driven "X"
off	off	no connection

 

- CMOS uses pFETs to implement the pullup network and nFETs to implement the pulldown network


Some Questionable Gates

 - What can go wrong with the following gates?



$A=0 \ B=1$ or $A=1 \ B=0$
connect supply and ground

short circuit

 


pFET doesn't pull down

V_{OUT} below V_{TH}


nFET doesn't pull up

V_{OUT} above $V_{DD} - V_{TH}$

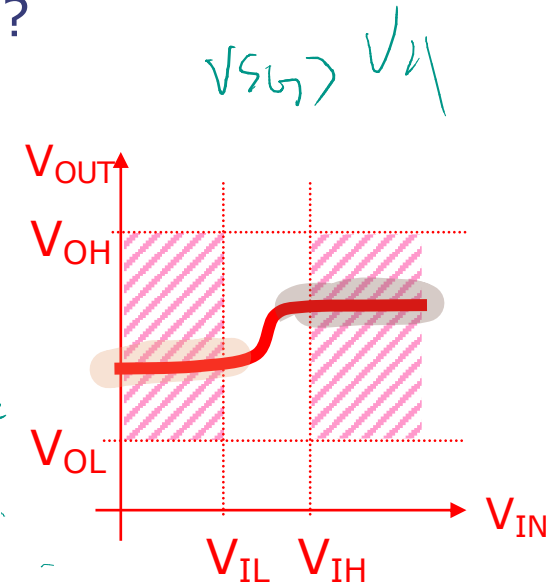


- CMOS Rule #1: Complementary pullup and pulldown networks
- CMOS Rule #2: pFETs in pullup, nFETs in pulldown


CMOS Complements

 


conducts when A is high

 


conducts when A is low: \bar{A}

 

 
conducts when A is high
and B is high: $A \cdot B$ *A+B*



 conducts when A is low
or B is low: $\bar{A} + \bar{B} = \overline{A \cdot B}$



 conducts when A is high
or B is high: $A + B$ *A+B*



conducts when A is low
and B is low: $\bar{A} \cdot \bar{B} = \overline{A + B}$

General CMOS Gate Recipe

Step 1. Derive the ^{p-FET} pullup network that does what you want, e.g.,

$$F = \bar{A} + \bar{B} \cdot \bar{C}$$




(Determine what combination of inputs generates a high output)

Step 2. Derive complementary pulldown network: replace pFETs with nFETs, series subnets with parallel subnets, and parallel subnets with series subnets

Step 3. Combine pFET pullup network from Step 1 with nFET pulldown network from Step 2 to form the CMOS gate.

Can CMOS gates implement arbitrary functions?

No

   

CMOS Gates are Inverting

- In a CMOS gate, rising inputs ($0 \rightarrow 1$) lead to falling outputs ($1 \rightarrow 0$) and vice versa
- On a rising input,
 - nFETs go OFF \rightarrow ON, so pulldown may connect output to ground
 - pFETs go ON \rightarrow OFF, so pullup may disconnect output from V_{DD}
 - Output either stays the same or falls
- Corollary: Cannot build non-inverting logic using a single CMOS gate
 - Example: AND


A	B	A·B
0	0	0
0	1	0
1	0	0
1	1	1

rising input rising output

Analyzing the Delay, Area, and Power of CMOS Gates


*NOTE: Demystification,
will not be on the quiz*

MOSFET Physical Structure

 


MOSFET Electrical View

 With $V_{GS} < V_{TH}$, almost no current flows between source and drain




 As V_{GS} reaches V_{TH} , a channel forms between source and drain



The shape of the channel (and its resistance) also depends on the voltage at the drain. But a low-resistance channel will exist while $V_{GS} > V_{TH}$




FET *First-Order* Electrical Model

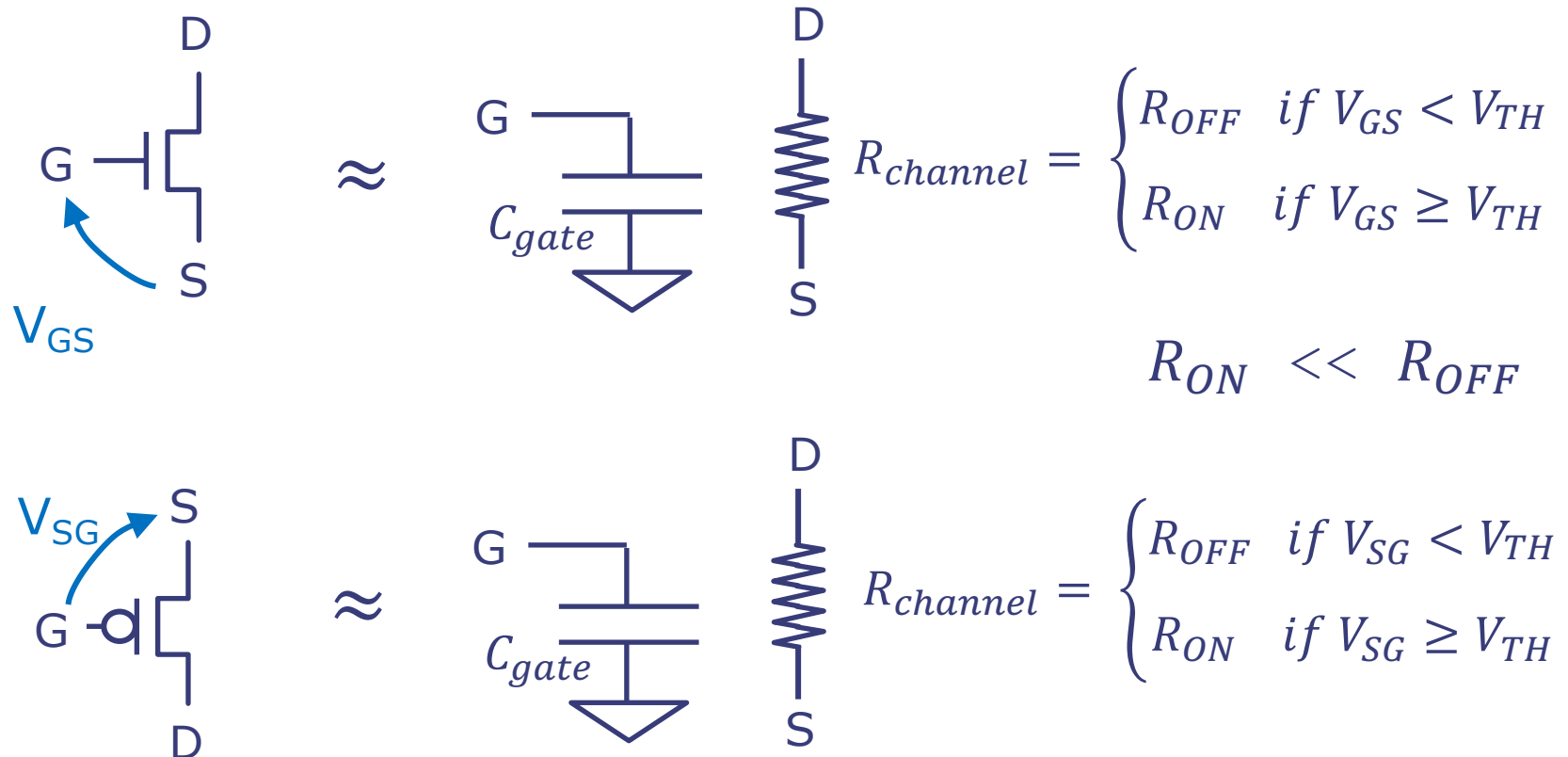

- Simplest possible model that lets us reason about delay, area, and power. Not very accurate!

CMOS Gate Delay

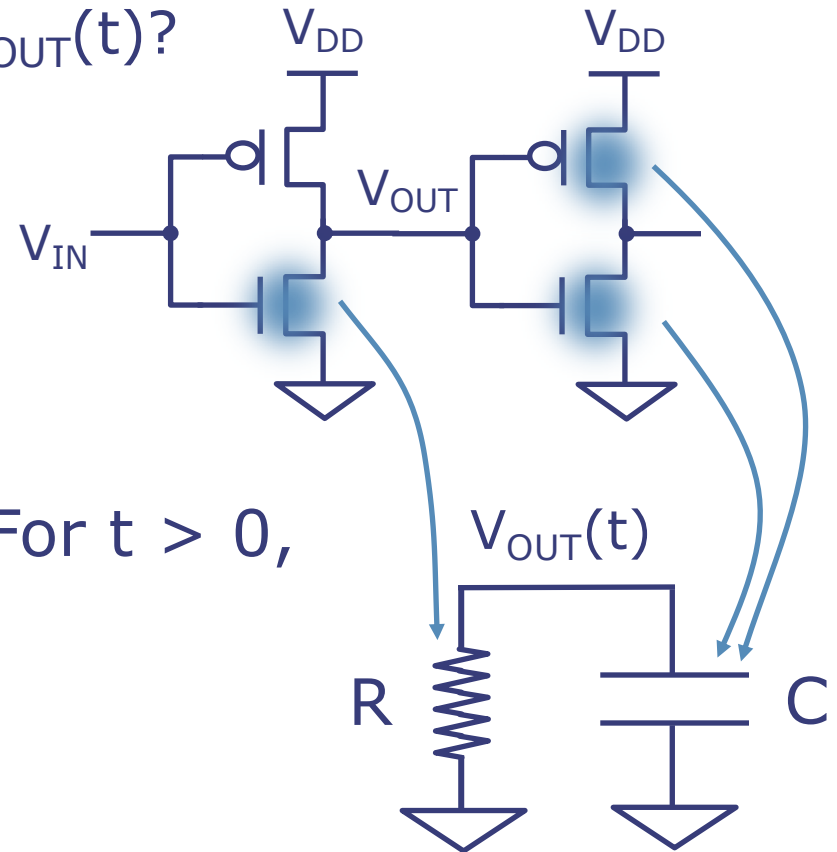  Consider the following circuit.
Given $V_{IN}(t)$, can you derive $V_{OUT}(t)$?




For $t > 0$,

$$V_{OUT}(t) = V_{OUT}(0)e^{-t/RC}$$

Propagation Delay

 
Propagation delay (t_{pD}): Upper bound on the delay from **valid inputs** to **valid outputs**.




To minimize t_{pD} , must keep resistances and capacitances low

Contamination Delay

 
Contamination delay (t_{CD}): Lower bound on the delay from any **invalid input** to an **invalid output**



MOSFET Sizing

 

\approx

 

How do C_{gate} and $R_{channel}$ change with L and W ?


$$C_{gate} \propto L \cdot W$$

$$R_{channel} \propto L/W$$

- CMOS gates use MOSFETs with smallest possible L and choose W to set performance
 - Wider FETs drive more current (lower R), but their gates are harder to drive (higher C) and they take more area


Standard Cell Libraries

 - A standard cell library provides implementations of common gates (NAND, NOR, XOR, etc.) for a specific implementation technology
- Each gate includes
 - Electrical parameters (e.g., R_s and C_s)
 - Physical layout
- Synthesis tools use gates from the standard library instead of sizing and placing individual transistors




Wide (High-Fanin) Gates

 Most standard cell libraries include 2-, 3- and 4-input devices:



But for a large number of inputs, the series connections of too many MOSFETs can lead to very large effective R_{pulldown} or R_{pullup} . Instead, use trees of smaller devices...

Example:
8-input
NAND

 

How does t_{PD} grow with the number of inputs N ?

If we use a single CMOS gate, $t_{PD} \propto N$

If we use a tree of gates, $t_{PD} \propto \log(N)$

CMOS Power Dissipation

耗散

- Total power dissipation: $P = P_{dynamic} + P_{static}$
- Dynamic power: Caused by $0 \leftrightarrow 1$ transitions of nodes in the circuit
 - Charging/discharging each capacitor consumes $\frac{1}{2}CV_{DD}^2$ energy
 - If on average C_S capacitance across the chip switches each cycle, and there are f_{CLK} cycles per second

$$P_{dynamic} = \frac{1}{2} C_S V_{DD}^2 f_{CLK}$$

or $\frac{Q}{T}$

- Static power: Caused by
 - Subthreshold leakage: Even when the FET is off, a very small current flows from source to drain ($R_{OFF} < \infty$)
 - Tunneling current: Gate and channel are separated by a very thin ($< 1\text{nm}$) dielectric, so some electrons tunnel through

$$P_{static} = I_{static} V_{DD}$$

- Static power is typically 10-30% of total power

Summary

- FETs behave as voltage-controlled switches
- CMOS gates:
 - Use complementary pullup and pulldown networks
 - Use pFETs in pullup, nFETs in pulldown network
- CMOS gates are inverting (rising inputs can only cause falling outputs, and vice versa)

Thank you!

Next lecture:
Combinational devices,
introduction to minispec